

56 Sparta Avenue • Newton, New Jersey 07860 (973) 300-3000 Sales • (973) 300-3600 Fax www.thorlabs.com



# ITC5052 - July 9, 2019

Item # ITC5052 was discontinued on July 9, 2019. For informational purposes, this is a copy of the website content at that time and is valid only for the stated product.

# LASER DIODE CURRENT / TEC CONTROLLER - ITC5000 SERIES

- Current & Temperature Control
- 3 Current Ranges
- Very Low Noise and Drift
- For All Laser Diode Polarities



ITC5000 & LS5000 Modules in TXP5016 Chassis



Easy-to-Use Graphical Interface (PC Not Included)

#### Hide Overview

# OVERVIEW

### Three Versions to Choose from:

- ITC5022: Laser Diode Current/TEC Controller ±200 mA / ±1.5 A
- ITC5052: Laser Diode Current/TEC Controller ±500 mA / ±1.5 A
- ITC5102: Laser Diode Current/TEC Controller ±1 A / ±1.5 A

#### **ITC5000** Features

- Laser Diode Current and Temperature Control
- Very Low Noise and Drift
- Excellent Temperature Stability
- Supports All Laser Diode and Monitor Diode Polarities
- · Constant Current (CC) and Constant Power (CP) Modes
- Superior Laser Diode Protection
- Internal & External Modulation
- Safe & Ultra-Stable Laser Diode Operation

#### Introduction

The **ITC5000 Series Modules** are combination laser diode and TEC controllers for the TXP platform. They allow space-saving simultaneous current and temperature control of a laser diode with a single module. The **ITC5000 Series** offers three laser diode current ranges,  $\pm 200 \text{ mA}$ ,  $\pm 500 \text{ mA}$  and  $\pm 1 \text{ A}$ , that support all laser diode and monitor diode polarities. These modules can also be modulated, externally or internally. All three models incorporate a TEC controller that provides up to  $\pm 1.5 \text{ A} / 5.25 \text{ W}$ .

#### Features

Besides common protection functions such as interlock and softstart, an advanced circuit design ensures that transient spikes cannot affect the laser current. The temperature controller, which is identical for all modules, is designed to keep the laser temperature constant for highly stable power and wavelength operation. Separate adjustment of the P, I and D shares of the temperature servo loop allow optimizing temperature settling times. An additional temperature window protection circuit switches the laser current off if the laser temperature leaves a preset temperature window.

The ITC5000 models offer exceptional noise and stability performance. All laser diode and photodiode pin configurations are supported.

#### Operation

For the operation of the **ITC5000** modules a TXP chassis is required. The modules are hot-pluggable, i.e. you can insert or remove them during operation of other modules. An intuitive graphical user interface (GUI) for the **ITC5000** is delivered with the TXP chassis, as well as drivers for LabVIEW<sup>™</sup>, LabWindows/CVI<sup>™</sup>, MSVC and Borland C.

#### **Connection Cables**

A CAB530 cable is required to connect the ITC5000 modules to a Thorlabs' Laser Diode Mount. The cable has to be ordered separately.

For further information, please contact our Tech Support Team.

Laser Diode Accessory Selection Guide						
Temperature Controlled Mounts	Passive Mounts	Passive Mounts with Collimation Package	Strain Relief Cables	Diode Sockets	Other Controllers	
	6	۵۵ 😄		*		

# Hide Specs


Item #	ITC5022	ITC5052	ITC5102	
Laser Controller: Current Control				
Control Range (continuous)	0 to ±200 mA	0 to ±500 mA	0 to ±1 A	
Compliance Voltage		>2.5 V (typ. >3 V)		
Resolution	4 µA	10 µA	20 µA	
Accuracy (typ., f.s.)	±100 µA	±250 µA	±1 mA	
Noise without Ripple (10Hz to 10MHz, RMS, typ.)	<2 µA	<7 μΑ	<20 µA	
Ripple (50Hz / 60Hz, RMS, typ.)		<0.5 µA		
Transients (Processor, typ.)	<15 µA	<30 µA	<50 µA	
Transients (other, typ.)	200 µA	500 µA	1 mA	
Drift (24hrs, at constant ambient temperature, typ.)	<2 µA	<5 μΑ	<20 µA	
Temperature Coefficient		<50 ppm/°C		
Laser Controller: Power Control				
Control Range of Photo Current		10 µA to 5 mA		
Resolution	0.1 µA			
Accuracy (typ., f.s.)	±5 μA			
Reverse Bias Voltage		0 to 4 V (adjustable)		
Laser Controller: Current Limit				
Setting Range	0 to >200 mA	0 to >500 mA	0 to >1 A	
Resolution	50 µA	125 µA	250 µA	
Accuracy (typ., f.s.)	±200 μA	±500 μA	±2 mA	
Laser Voltage Measurement				
Measurement Principle	4-Wire (improve	s accuracy by compensating for	r cable resistance)	
Measurement Range		0 to 4 V		
Resolution		0.15 mV		
Accuracy		±5 mV		
External Laser Modulation				

50 mA/V ± 10% 200 kHz	100 mA/V ± 10%		
200 kHz			
200 kHz			
0.5 mA/V ± 10%			
Sinusoidal, Triangular, Squ	are		
0.02 to 20 kHz			
4 µs			
-1.5 A to +1.5 A			
>3.5 V			
5.25 W			
60 µA			
-4 V to +4 V			
0.2 mV			
<1 mA			
Thermistor			
0.2 to 40 kΩ			
0.8 Ω			
±10 Ω			
1 Ω			
PID, analog			
12 Bit each			
0 to >1.5 A			
0.5 mA			
±20 mA			
Global and Local Interloc			
· ·	,		
	-		
· ·			
	m <sup>3</sup>		
	0.5 mA ±20 mA		

Hide Pin Diagrams

PIN DIAGRAMS

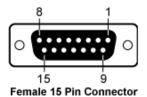Laser Diode, Monitor Diode, TEC and Thermistor Connection



Pin	Connection	Pin	Connection
1	Interlock/Status LED (LED_ILK)	9	Laser Diode Voltage Measurement (ULD-)
2	Monitor Diode Ground/Bias Ground (PD_GND)		Laser Diode Cathode (LDK)
3	3 Laser Diode Ground (LGND)		Laser Diode Anode (LDA)
4	Monitor Diode Anode or Cathode, Bias Out (PD_BIAS)	12	Laser Diode Voltage Measurement (ULD+)
5	5 Interlock Ground (DGND)		TEC Voltage Measurement (-) UTEC-
6	6 TEC Voltage Measurement (+) UTEC+		Thermistor Ground (TH-)
7	TEC Plus (TEC +)	15	Thermister (THT)
8	TEC Minus (Ground) (TEC -)	15	Thermistor (TH+)


**External Modulation via SMA** 

# SMA Female



Voltage Range 0 - 10 V

# Hide Software

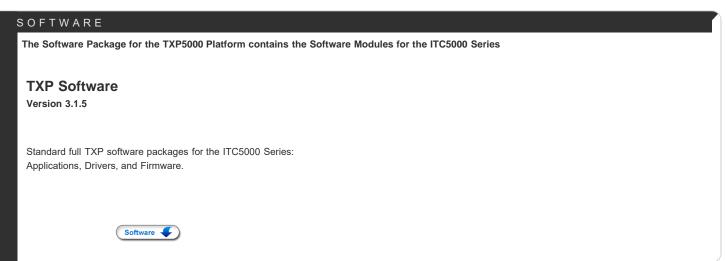


# Hide Shipping List

SHIPPING LIST				
	ITC5022	ITC5052	ITC5102	Part
	х			Laser Diode Current/TEC Controller ±200 mA / ±1.5 A (ITC5022)
		х		Laser Diode Current/TEC Controller ±500 mA / ±1.5 A (ITC5052)
			х	Laser Diode Current/TEC Controller ±1 A / ±1.5 A (ITC5102)
	х	х	х	Operating Manual

#### PID TUTORIAL
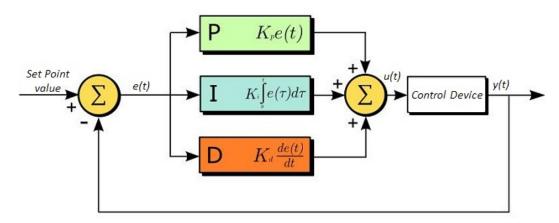
# **PID Basics**

The PID circuit is often utilized as a control loop feedback controller and is very commonly used for many forms of servo circuits. The letters making up the acronym PID correspond to Proportional (P), Integral (I), and Derivative (D), which represents the three control settings of a PID circuit. The purpose of any servo circuit is to hold the system at a predetermined value (set point) for long periods of time. The PID circuit actively controls the system so as to hold it at the set point by generating an error signal that is essentially the difference between the set point and the current value. The three controls relate to the time-dependent error signal; at its simplest, this can be thought of as follows: Proportional is dependent upon the present error, Integral is dependent upon the accumulation of past error, and Derivative is the prediction of future error. The results of each of the controls are then fed into a weighted sum, which then adjusts the output of the circuit, u(t). This output is fed into a control device, its value is fed back into the circuit, and the process is allowed to actively stabilize the circuit's output to reach and hold at the set point value. The block diagram below illustrates very simply the action of a PID circuit. One or more of the controls can be utilized in any servo circuit depending on system demand and requirement (i.e., P, I, PI, PD, or PID).



Through proper setting of the controls in a PID circuit, relatively quick response with minimal overshoot (passing the set point value) and ringing (oscillation about the set point value) can be achieved. Let's take as an example a temperature servo, such as that for temperature stabilization of a laser diode. The PID circuit will ultimately servo the current to a Thermo Electric Cooler (TEC) (often times through control of the gate voltage on an FET). Under this example, the current is referred to as the Manipulated Variable (MV). A thermistor is used to monitor the temperature of the laser diode, and the voltage over the thermistor is used as the Process Variable (PV). The Set Point (SP) voltage is set to correspond to the desired temperature. The error signal, e(t), is then just the difference between the SP and PV. A PID controller will generate the error signal and then change the MV to reach the desired result. If, for instance, e(t) states that the laser diode is too hot, the circuit will allow more current to flow through the TEC (proportional control). Since proportional control is proportional to e(t), it may not cool the laser diode quickly enough. In that event, the circuit will further increase the amount of current through the TEC (integral control) by looking at the previous errors and adjusting the output in order to reach the desired value. As the SP is reached [e(t) approaches zero], the circuit will decrease the current through the TEC in anticipation of reaching the SP (derivative control).

Please note that a PID circuit will not guarantee optimal control. Improper setting of the PID controls can cause the circuit to oscillate significantly and lead to instability in control. It is up to the user to properly adjust the PID gains to ensure proper performance.


# **PID Theory**

The output of the PID control circuit, u(t), is given as

$$u(t) = MV(t) = K_p e(t) + K_i \int_0^t e(\tau) d\tau + K_d \frac{d}{dt} e(t)$$

where  $K_p$ = Proportional Gain  $K_i$  = Integral Gain  $K_d$  = Derivative Gain e(t) = SP - PV(t)

 
From here we can define the control units through their mathematical definition and discuss each in a little more detail. Proportional control is proportional to the error signal; as such, it is a direct response to the error signal generated by the circuit:



Larger proportional gain results is larger changes in response to the error, and thus affects the speed at which the controller can respond to changes in the

system. While a high proportional gain can cause a circuit to respond swiftly, too high a value can cause oscillations about the SP value. Too low a value and the circuit cannot efficiently respond to changes in the system.

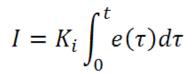
Integral control goes a step further than proportional gain, as it is proportional to not just the magnitude of the error signal but also the duration of the error.



Integral control is highly effective at increasing the response time of a circuit along with eliminating the steady-state error associated with purely proportional control. In essence integral control sums over the previous error, which was not corrected, and then multiplies that error by K<sub>i</sub> to produce the integral

response. Thus, for even small sustained error, a large aggregated integral response can be realized. However, due to the fast response of integral control, high gain values can cause significant overshoot of the SP value and lead to oscillation and instability. Too low and the circuit will be significantly slower in responding to changes in the system.

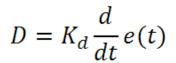Derivative control attempts to reduce the overshoot and ringing potential from proportional and integral control. It determines how quickly the circuit is changing over time (by looking at the derivative of the error signal) and multiplies it by  $K_d$  to produce the derivative response.



Unlike proportional and integral control, derivative control will slow the response of the circuit. In doing so, it is able to partially compensate for the overshoot as well as damp out any oscillations caused by integral and proportional control. High gain values cause the circuit to respond very slowly and can leave one susceptible to noise and high frequency oscillation (as the circuit becomes too slow to respond quickly). Too low and the circuit is prone to overshooting the SP value. However, in some cases overshooting the SP value by any significant amount must be avoided and thus a higher derivative gain (along with lower proportional gain) can be used. The chart below explains the effects of increasing the gain of any one of the parameters independently.

Parameter Increased	Rise Time	Overshoot	Settling Time	Steady-State Error	Stability
К <sub>р</sub>	Decrease	Increase	Small Change	Decrease	Degrade
κ <sub>i</sub>	Decrease	Increase	Increase	Decrease Significantly	Degrade
K <sub>d</sub>	Minor Decrease	Minor Decrease	Minor Decrease	No Effect	Improve (for small K <sub>d</sub> )

#### Tuning

In general the gains of P, I, and D will need to be adjusted by the user in order to best servo the system. While there is not a static set of rules for what the values should be for any specific system, following the general procedures should help in tuning a circuit to match one's system and environment. In general a PID circuit will typically overshoot the SP value slightly and then quickly damp out to reach the SP value.

Manual tuning of the gain settings is the simplest method for setting the PID controls. However, this procedure is done actively (the PID controller turned on and properly attached to the system) and requires some amount of experience to fully integrate. To tune your PID controller manually, first the integral and derivative gains are set to zero. Increase the proportional gain until you observe oscillation in the output. Your proportional gain should then be set to roughly half this value. After the proportional gain is set, increase the integral gain until any offset is corrected for on a time scale appropriate for your system. If you increase this gain too much, you will observe significant overshoot of the SP value and instability in the circuit. Once the integral gain is set, the derivative gain can then be increased. Derivative gain will reduce overshoot and damp the system quickly to the SP value. If you increase the derivative gain too much, you will see large overshoot (due to the circuit being too slow to respond). By playing with the gain settings, you can maximize the performance of your PID circuit, resulting in a circuit that quickly responds to changes in the system and effectively damps out oscillation about the SP value.

While manual tuning can be very effective at setting a PID circuit for your specific system, it does require some amount of experience and understanding of PID circuits and response. The Ziegler-Nichols method for PID tuning offers a bit more structured guide to setting PID values. Again, you'll want to set the integral and derivative gain to zero. Increase the proportional gain until the circuit starts to oscillate. We will call this gain level  $K_u$ . The oscillation will have a period of  $P_u$ . Gains are for various control circuits are then given below in the chart.

Control Type	К <sub>р</sub>	K <sub>i</sub>	K <sub>d</sub>
Р	0.50 K <sub>u</sub>	-	-
PI	0.45 K <sub>u</sub>	1.2 K <sub>p</sub> /P <sub>u</sub>	-
PID	0.60 K <sub>u</sub>	2 K <sub>p</sub> /P <sub>u</sub>	K <sub>p</sub> P <sub>u</sub> /8

Part Number	Description	Price	Availability
ITC5022	Laser Diode Current/TEC Controller ±200mA / 1.5A	\$2,257.74	Lead Time
ITC5052	Laser Diode Current/TEC Controller ±500mA / 1.5A	\$2,257.74	Lead Time
ITC5102	Laser Diode Current/TEC Controller ±1A / 1.5A	\$2,257.74	Lead Time

# Hide Connection Cable for the ITC5000 Series

Pin #	CAB530 (15 Pin)	CAB530 (9 Pin)	CAB530 (9 Pin)
1	9 Male 15 Pin Connector	1 5 0 0 0 0 6 9 Male 9 Pin Connector	Female 9 Pin Connector
1	Interlock and Status LASER ON/OFF	Interlock and Status LASER ON/OFF	N.C.
2	Photodiode Ground, Cathode or Anode (configurable)	Photodiode Ground, Cathode or Anode (configurable)	Thermistor (+)
3	Laser Diode Ground	Laser Diode Ground	Thermistor (-), Ground
4	Photodiode Input, Anode or Cathode (configurable)	Photodiode Input, Anode or Cathode (configurable)	TEC (+)
5	Ground for Pin 1	Ground for Pin 1	TEC (-), Status LED (-)
6	Voltage Measurement TEC (+)	Voltage Measurement Laser Diode Cathode	N.C.
7	TEC (+)	Laser Diode Cathode (with Polarity Anode Grounded - AG)	N.C.
8	TEC (-)	Laser Diode Anode (with Polarity Cathode Grounded - CG)	N.C.
9	Voltage Measurement Laser Diode Cathode	Voltage Measurement Laser Diode Anode	N.C.
10	Laser Diode Cathode (with Polarity Anode Grounded - AG)		
11	Laser Diode Anode (with Polarity Cathode Grounded - CG)		
12	Voltage Measurement Laser Diode Anode		
13	Voltage Measurement TEC (-)		
14	Thermistor (-), Ground		
15	Thermistor (+)		

Part Number	Description	Price	Availability
CAB530 C	Cable for a ITC5000 series card to Thorlabs TEC Laser Diode Mounts	\$102.96	Today